


ECE380 Digital Logic

Implementation Technology:
Look-up Tables, XOR and XNOR
gates

Look-up tables


- A logic block commonly used in FPGA devices is the **look-up table** (LUT)
- An LUT contains **storage cells** that are used to implement small logic functions
- Each cell is capable of storing a single logic value (0 or 1)
- Multiplexers are used to select one of the storage cells for output
- Essentially, the cells store the truth table for a function and the multiplexers select a particular cell for output based on a set of select (control) inputs

Two-input LUT structure

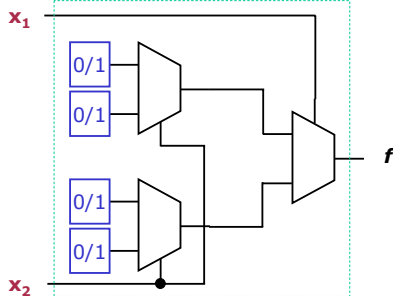


Programmed LUT ($f=a'b+ab'$)

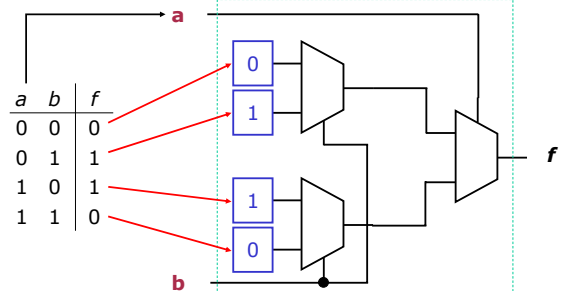most significant variable
controls last multiplexer



Three-input LUT structure

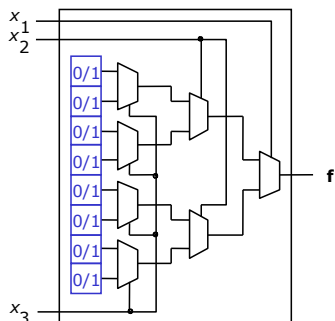


Three-input LUT example

- Show the diagram for a programmed LUT that implements the function
- $f(a,b,c)=a'bc+abc'+ac$

Exclusive OR (XOR) gate


- Another basic element, very useful in building circuits that perform arithmetic operations, is the exclusive OR (XOR) gate
- XOR function is denoted with the \oplus symbol
- In SOP form, $a \oplus b = ab' + a'b$
- Output is '1' only if the inputs are different

a	b	$a \oplus b$
0	0	0
0	1	1
1	0	1
1	1	0

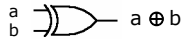

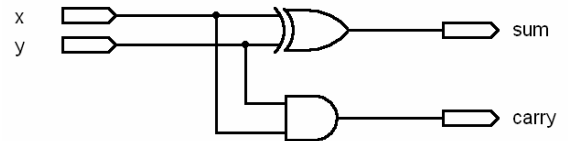Example XOR usage

- Recall the adder circuit
 - $\text{sum} = xy' + x'y$
 - $\text{carry} = xy$



XOR of three variables


- What is the canonical SOP form for the following expression?

$$f(a,b,c) = a \oplus b \oplus c$$

Exclusive NOR (XNOR) gate

- Derived from the XOR function, XNOR is the complement of XOR
- XNOR function is denoted with the \equiv symbol
- In SOP form, $a \equiv b = (a \oplus b)' = ab + a'b'$
- Output is '1' only if the inputs are the same
- Also called an equivalence function

a	b	$a \equiv b$
0	0	1
0	1	0
1	0	0
1	1	1

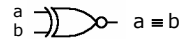

XNOR of three variables

- What is the canonical SOP form for the following expression?

$$f(a,b,c) = a \equiv b \equiv c$$